

Combinational Circuit Example (4A)

Copyright (c) 2025-2011 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Boolean functions of **a** and **b**

What are these?

$$\bar{a} \cdot \bar{b}$$

$$\bar{a} \cdot b$$

$$a \cdot \bar{b}$$

$$a \cdot b$$

Consider them as a function

$$f_0(a, b) = \bar{a} \cdot \bar{b}$$

$$f_1(a, b) = \bar{a} \cdot b$$

$$f_2(a, b) = a \cdot \bar{b}$$

$$f_3(a, b) = a \cdot b$$

Boolean Function Definition for $f_i = 1$

$$f_0(a,b) = \bar{a} \cdot \bar{b}$$

a	b	f_0
0	0	1
0	1	0
1	0	0
1	1	0



$$\bar{a} \cdot \bar{b} = 1 \iff (\bar{a}=1) \wedge (\bar{b}=1)$$

$$\bar{a} \cdot \bar{b} = 1 \text{ when } (a=0) \wedge (b=0)$$

$\bar{a} \cdot \bar{b} = 0$
for other three cases

$$f_1(a,b) = \bar{a} \cdot b$$

a	b	f_1
0	0	0
0	1	1
1	0	0
1	1	0



$$\bar{a} \cdot b = 1 \iff (\bar{a}=1) \wedge (b=1)$$

$$\bar{a} \cdot b = 1 \text{ when } (a=0) \wedge (b=1)$$

$\bar{a} \cdot b = 0$
for other three cases

$$f_2(a,b) = a \cdot \bar{b}$$

a	b	f_2
0	0	0
0	1	0
1	0	1
1	1	0



$$a \cdot \bar{b} = 1 \iff (a=1) \wedge (\bar{b}=1)$$

$$a \cdot \bar{b} = 1 \text{ when } (a=1) \wedge (b=0)$$

$a \cdot \bar{b} = 0$
for other three cases

$$f_3(a,b) = a \cdot b$$

a	b	f_3
0	0	0
0	1	0
1	0	0
1	1	1



$$a \cdot b = 1 \iff (a=1) \wedge (b=1)$$

$$a \cdot b = 1 \text{ when } (a=1) \wedge (b=1)$$

$a \cdot b = 0$
for other three cases

Alternative Boolean Function Definition (1)

$$f_0(a,b) = \bar{a} \cdot \bar{b}$$

a	b	f_0
0	0	1
0	1	0
1	0	0
1	1	0

$$(a+\bar{b}) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$$

a	b	$(a+\bar{b}) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$
0	0	$(0+\bar{0}) \cdot (\bar{0}+0) \cdot (\bar{0}+\bar{0})=1$
0	1	$(0+\bar{1}) \cdot (\bar{0}+1) \cdot (\bar{0}+\bar{1})=0$
1	0	$(1+\bar{0}) \cdot (\bar{1}+0) \cdot (\bar{1}+\bar{0})=0$
1	1	$(1+\bar{1}) \cdot (\bar{1}+1) \cdot (\bar{1}+\bar{1})=0$

$$f_0(a,b) = \bar{a} \cdot \bar{b}$$

$$= (a+\bar{b}) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$$

$$f_1(a,b) = \bar{a} \cdot b$$

a	b	f_1
0	0	0
0	1	1
1	0	0
1	1	0

$$(a+b) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$$

a	b	$(a+b) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$
0	0	$(0+0) \cdot (\bar{0}+0) \cdot (\bar{0}+\bar{0})=0$
0	1	$(0+1) \cdot (\bar{0}+1) \cdot (\bar{0}+\bar{1})=1$
1	0	$(1+0) \cdot (\bar{1}+0) \cdot (\bar{1}+\bar{0})=0$
1	1	$(1+1) \cdot (\bar{1}+1) \cdot (\bar{1}+\bar{1})=0$

$$f_1(a,b) = \bar{a} \cdot b$$

$$= (a+b) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$$

$$f_2(a,b) = a \cdot \bar{b}$$

a	b	f_2
0	0	0
0	1	0
1	0	1
1	1	0

$$(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+\bar{b})$$

a	b	$(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+\bar{b})$
0	0	$(0+0) \cdot (0+\bar{0}) \cdot (\bar{0}+\bar{0})=0$
0	1	$(0+1) \cdot (0+\bar{1}) \cdot (\bar{0}+\bar{1})=0$
1	0	$(1+0) \cdot (1+\bar{0}) \cdot (\bar{1}+\bar{0})=1$
1	1	$(1+1) \cdot (1+\bar{1}) \cdot (\bar{1}+\bar{1})=0$

$$f_2(a,b) = a \cdot \bar{b}$$

$$= (a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+\bar{b})$$

$$f_3(a,b) = a \cdot b$$

a	b	f_3
0	0	0
0	1	0
1	0	0
1	1	1

$$(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+b)$$

a	b	$(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+b)$
0	0	$(0+0) \cdot (0+\bar{0}) \cdot (\bar{0}+0)=0$
0	1	$(0+1) \cdot (0+\bar{1}) \cdot (\bar{0}+1)=0$
1	0	$(1+0) \cdot (1+\bar{0}) \cdot (\bar{1}+0)=0$
1	1	$(1+1) \cdot (1+\bar{1}) \cdot (\bar{1}+1)=1$

$$f_3(a,b) = a \cdot b$$

$$= (a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+b)$$


Alternative Boolean Function Definition (2)

$f_0(a,b) = \bar{a} \cdot \bar{b}$	$f_1(a,b) = \bar{a} \cdot b$	$f_2(a,b) = a \cdot \bar{b}$	$f_3(a,b) = a \cdot b$	⇒ 1
$\bar{a} \cdot \bar{b} = 1 \iff$ $(\bar{a}=1) \wedge (\bar{b}=1)$	$\bar{a} \cdot b = 1 \iff$ $(\bar{a}=1) \wedge (b=1)$	$a \cdot \bar{b} = 1 \iff$ $(a=1) \wedge (\bar{b}=1)$	$a \cdot b = 1 \iff$ $(a=1) \wedge (b=1)$	
$\bar{a} \cdot \bar{b} = 1$ when $(a=0) \wedge (b=0)$	$\bar{a} \cdot b = 1$ when $(a=0) \wedge (b=1)$	$a \cdot \bar{b} = 1$ when $(a=1) \wedge (b=0)$	$a \cdot b = 1$ when $(a=1) \wedge (b=1)$	
$f_0(a,b) =$ $(a+\bar{b}) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$	$f_1(a,b) =$ $(a+b) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$	$f_2(a,b) =$ $(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+\bar{b})$	$f_3(a,b) =$ $(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+b)$	⇒ 0
$(a+\bar{b}) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b}) = 0 \iff$ $(a+\bar{b}=0) \vee (\bar{a}+b=0) \vee (\bar{a}+\bar{b}=0)$	$(a+b) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b}) = 0 \iff$ $(a+b=0) \vee (\bar{a}+b=0) \vee (\bar{a}+\bar{b}=0)$	$(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+\bar{b}) = 0 \iff$ $(a+b=0) \vee (a+\bar{b}=0) \vee (\bar{a}+\bar{b}=0)$	$(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+b) = 0 \iff$ $(a+b=0) \vee (a+\bar{b}=0) \vee (\bar{a}+b=0)$	
$\bar{a} \cdot \bar{b} = 0$ when $[(a=0) \wedge (b=1)] \vee$ $[(a=1) \wedge (b=0)] \vee$ $[(a=1) \wedge (b=1)]$	$\bar{a} \cdot b = 0$ when $[(a=0) \wedge (b=0)] \vee$ $[(a=1) \wedge (b=0)] \vee$ $[(a=1) \wedge (b=1)]$	$a \cdot \bar{b} = 0$ $[(a=0) \wedge (b=0)] \vee$ $[(a=0) \wedge (b=1)] \vee$ $[(a=1) \wedge (b=1)]$	$a \cdot b = 0$ $[(a=0) \wedge (b=0)] \vee$ $[(a=0) \wedge (b=1)] \vee$ $[(a=1) \wedge (b=0)]$	

Boolean Function Definition for $f_i = 0$

$$f_0(a,b) = (a+b) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$$

a	b	f_1
0	0	1
0	1	0
1	0	0
1	1	0

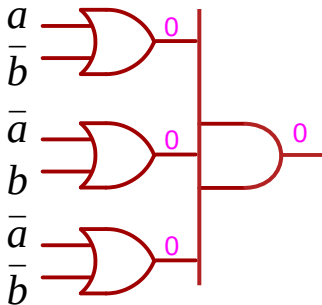

$$(a+\bar{b}) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b}) = 0$$

$$(a+\bar{b}=0) \vee (\bar{a}+b=0) \vee (\bar{a}+\bar{b}=0)$$


$$(a=0 \wedge b=1) \vee$$

$$(a=1 \wedge b=0) \vee$$

$$(a=1 \wedge b=1)$$

$$f_1(a,b) = (a+b) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b})$$

a	b	f_2
0	0	0
0	1	1
1	0	0
1	1	0

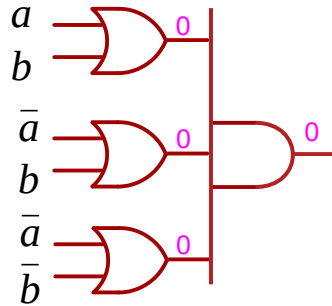

$$(a+b) \cdot (\bar{a}+b) \cdot (\bar{a}+\bar{b}) = 0$$

$$(a+b=0) \vee (\bar{a}+b=0) \vee (\bar{a}+\bar{b}=0)$$


$$(a=0 \wedge b=0) \vee$$

$$(a=1 \wedge b=0) \vee$$

$$(a=1 \wedge b=1)$$

$$f_2(a,b) = (a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+\bar{b})$$

a	b	f_3
0	0	0
0	1	0
1	0	1
1	1	0

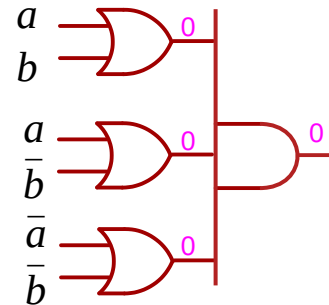

$$(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+\bar{b}) = 0$$

$$(a+b=0) \vee (a+\bar{b}=0) \vee (\bar{a}+\bar{b}=0)$$


$$(a=0 \wedge b=0) \vee$$

$$(a=0 \wedge b=1) \vee$$

$$(a=1 \wedge b=1)$$

$$f_3(a,b) = (a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+b)$$

a	b	f_4
0	0	0
0	1	0
1	0	0
1	1	1

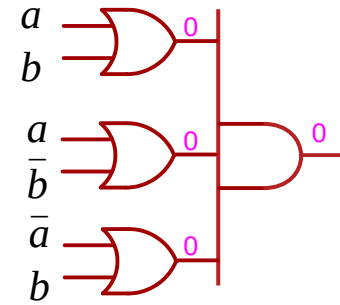

$$(a+b) \cdot (a+\bar{b}) \cdot (\bar{a}+b) = 0$$

$$(a+b=0) \vee (a+\bar{b}=0) \vee (\bar{a}+b=0)$$

$$(a=0 \wedge b=0) \vee$$

$$(a=0 \wedge b=1) \vee$$

$$(a=1 \wedge b=0)$$

Logic gates in terms of $\mathbf{f_i}$

Use $\mathbf{f_0, f_1, f_2, f_3}$ to express logic gates

$$a \cdot b$$



a	b	•
0	0	0
0	1	0
1	0	0
1	1	1

$$a \cdot b = f_3$$

$$a + b$$



a	b	+
0	0	0
0	1	1
1	0	1
1	1	1

$$a + b = f_1 + f_2 + f_3$$

$$a + b = a \oplus b + a \cdot b$$

$$a \oplus b$$



a	b	$\oplus$
0	0	0
0	1	1
1	0	1
1	1	0

$$a \oplus b = f_1 + f_2$$

$$\overline{a \oplus b}$$



a	b	$\oplus$
0	0	1
0	1	0
1	0	0
1	1	1

$$\overline{a \oplus b} = f_0 + f_3$$

XOR gate in terms of f_i

Use f_1, f_2 to express an XOR logic gate

$$a \oplus b$$

a	b	$\oplus$
0	0	0
0	1	1
1	0	1
1	1	0

=

$$f_1(a,b) = \bar{a} \cdot b$$

a	b	f_1
0	0	0
0	1	1
1	0	0
1	1	0

+

$$f_2(a,b) = a \cdot \bar{b}$$

a	b	f_2
0	0	0
0	1	0
1	0	1
1	1	0




defined by the truth table

$$a \oplus b = 1 \iff (a=1 \wedge b=0) \vee (a=0 \wedge b=1)$$

$$\begin{aligned} \bar{a} \cdot b + a \cdot \bar{b} &= 1 \iff \\ (\bar{a} \cdot b = 1) \vee (a \cdot \bar{b} = 1) &\iff \\ (a=0 \wedge b=1) \vee (a=1 \wedge b=0) \end{aligned}$$

combined by the minterms

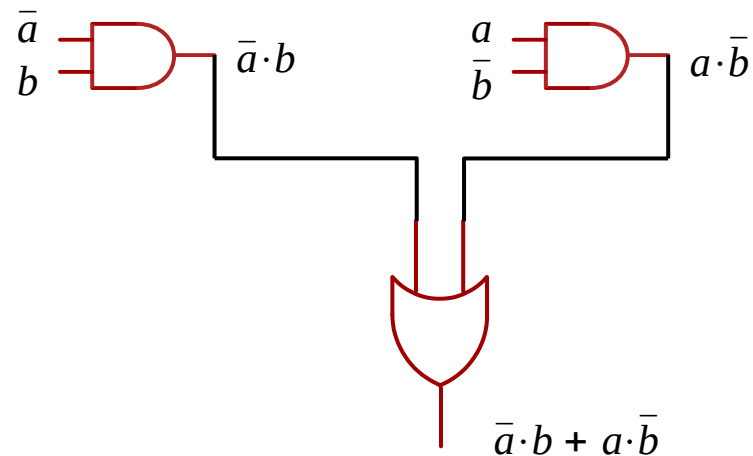

XNOR gate in terms of f_i

Use f_0, f_3 to express an XNOR logic gate

$$a \oplus b$$

a	b	$\oplus$
0	0	0
0	1	1
1	0	1
1	1	0

=

$$f_0(a,b) = \bar{a} \cdot \bar{b}$$

a	b	f_0
0	0	1
0	1	0
1	0	0
1	1	0

+

$$f_3(a,b) = a \cdot b$$

a	b	f_3
0	0	0
0	1	0
1	0	0
1	1	1




defined by the truth table

$$\begin{aligned} \bar{a \oplus b} &= 1 \iff \\ (a=0 \wedge b=0) \vee (a=1 \wedge b=1) \end{aligned}$$

$$\begin{aligned} \bar{a} \cdot \bar{b} + a \cdot b &= 1 \iff \\ (\bar{a} \cdot \bar{b}=1) \vee (a \cdot b=1) &\iff \\ (a=0 \wedge b=0) \vee (a=1 \wedge b=1) \end{aligned}$$

combined by the minterms

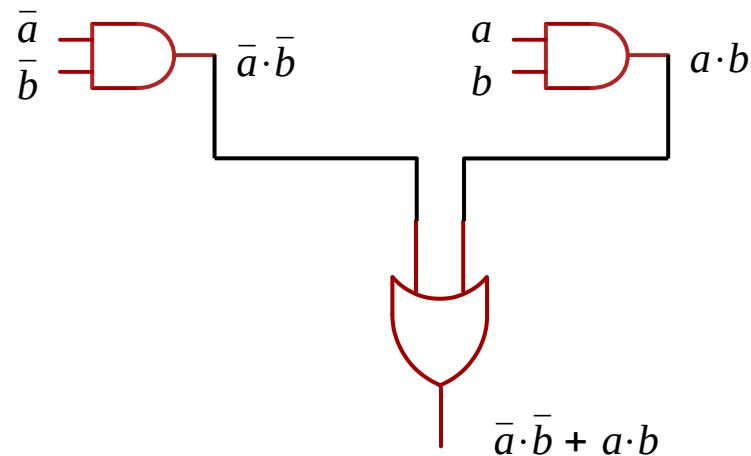

OR gate in terms of f_i

Use f_1, f_2, f_3 to express an OR logic gate

$$a+b$$

a	b	+
0	0	0
0	1	1
1	0	1
1	1	1

=

$$f_1(a,b) = \bar{a} \cdot b$$

a	b	f_1
0	0	0
0	1	1
1	0	0
1	1	0

+

$$f_2(a,b) = a \cdot \bar{b}$$

a	b	f_2
0	0	0
0	1	0
1	0	1
1	1	0

+

$$f_3(a,b) = a \cdot b$$

a	b	f_3
0	0	0
0	1	0
1	0	0
1	1	1




defined by the truth table


$$a+b = 1 \iff (a=0 \wedge b=1) \vee (a=1 \wedge b=0) \vee (a=1 \wedge b=1)$$

$$\begin{aligned} \bar{a} \cdot b + a \cdot \bar{b} + a \cdot b &= 1 \iff \\ (\bar{a} \cdot b = 1) \vee (a \cdot \bar{b} = 1) \vee (a \cdot b = 1) &\iff \\ (a=0 \wedge b=1) \vee (a=1 \wedge b=0) \vee (a=1 \wedge b=1) \end{aligned}$$

combined by the minterms

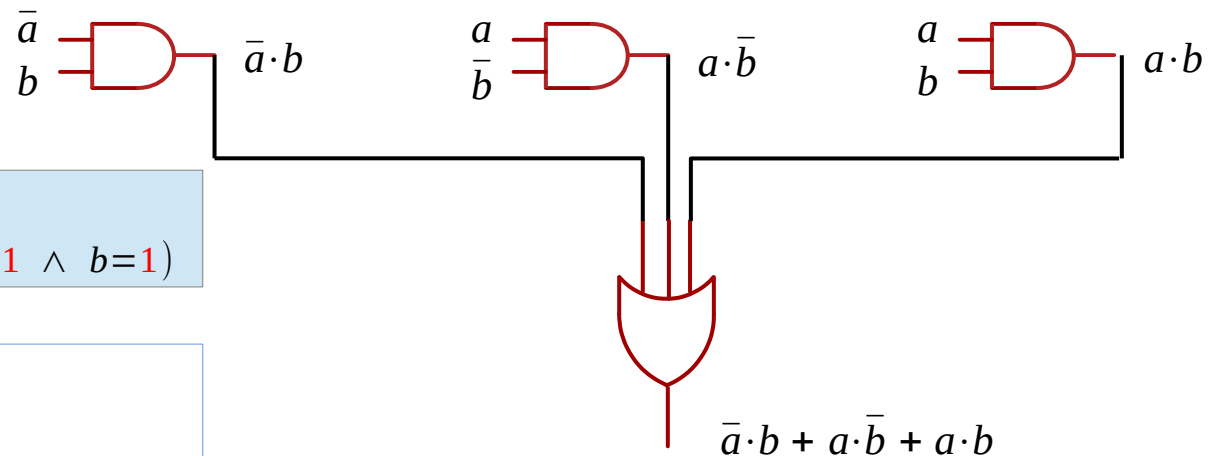

Adding three 1-bit numbers

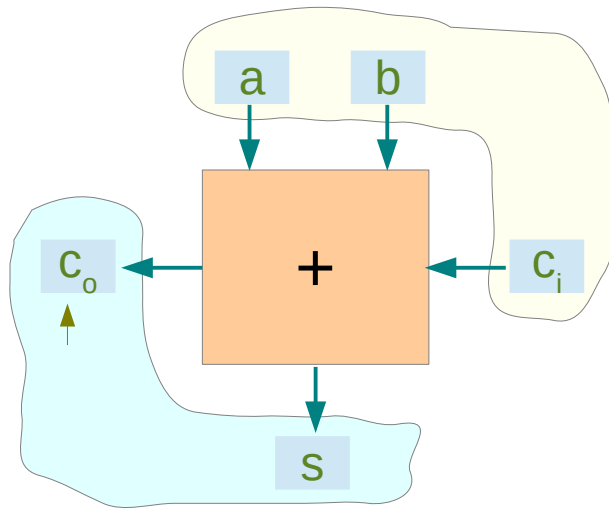

no binary position assumed


0	0	0	1
0	1	0	1
+	0	0	0
0	0	0	1
0	1	1	0

a	
b	
+	ci
co	s

implicit binary position

0	0	1	1
0	1	0	1
+	1	1	1
0	1	1	0
1	0	0	1

A 4-bit adder

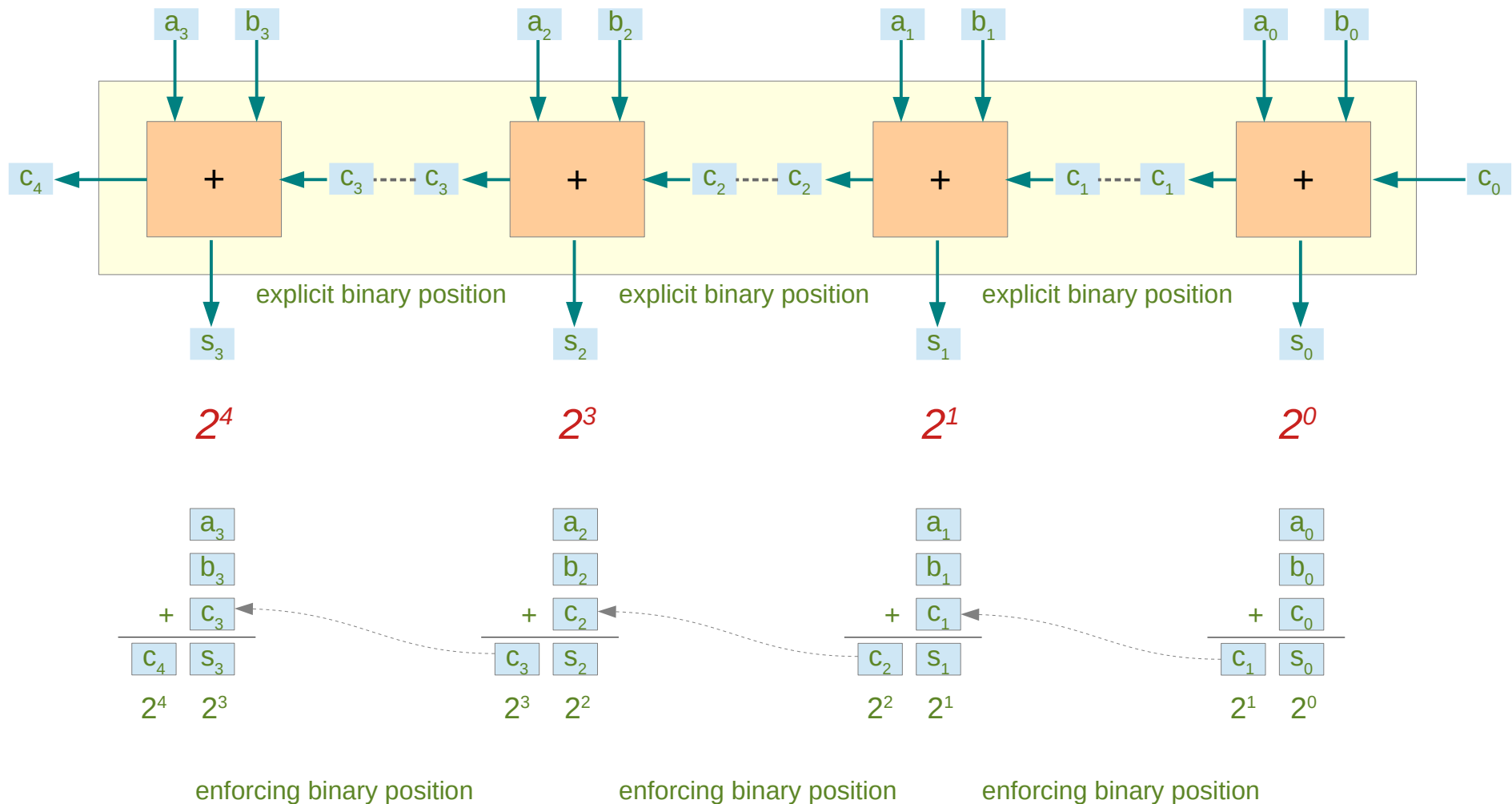

K-maps for output c_o and s

a	b	c_i	c_o
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

inputs

		c_o			
c_i	a b	00	01	11	10
	0	0	0	1	0
1	0	0	1	1	1

a	b	c_i	s
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

inputs

		s			
c_i	a b	00	01	11	10
	0	0	1	0	1
1	0	1	0	1	0

$$\begin{aligned}
 c_o &= \bar{a} \cdot b \cdot c_i + a \cdot \bar{b} \cdot c_i + a \cdot b \cdot \bar{c}_i + a \cdot b \cdot c_i \\
 &= a \cdot b + b \cdot c_i + c_i \cdot a \quad \text{by the K-map simplification}
 \end{aligned}$$

$$\begin{aligned}
 c_o &= (\bar{a} \cdot b + a \cdot \bar{b}) \cdot c_i + (a \cdot b) \cdot (\bar{c}_i + c_i) \\
 &= (a \oplus b) \cdot c_i + a \cdot b \quad \text{by the insight}
 \end{aligned}$$


$$s = \bar{a} \cdot \bar{b} \cdot c_i + \bar{a} \cdot b \cdot \bar{c}_i + a \cdot \bar{b} \cdot \bar{c}_i + a \cdot b \cdot c_i$$

Hand minimization for the output c_o and s


$$\begin{aligned}
 c_o &= a \cdot b + b \cdot c_i + c_i \cdot a \\
 &= a \cdot b + (a + b) \cdot c_i \quad a+b = m_1+m_2+m_3 \text{ minterms} \\
 &= a \cdot b + (a \cdot \bar{b} + \bar{a} \cdot b + a \cdot b) \cdot c_i \\
 &= a \cdot b + a \cdot b \cdot c_i + (a \cdot \bar{b} + \bar{a} \cdot b) \cdot c_i \\
 &= a \cdot b \cdot (1 + c_i) + (a \oplus b) \cdot c_i \\
 &= a \cdot b + (a \oplus b) \cdot c_i
 \end{aligned}$$

$$\begin{aligned}
 s &= \bar{a} \cdot \bar{b} \cdot c_i + \bar{a} \cdot b \cdot \bar{c}_i + a \cdot \bar{b} \cdot \bar{c}_i + a \cdot b \cdot c_i \\
 &= \bar{a} \cdot \bar{b} \cdot c_i + a \cdot b \cdot c_i + \bar{a} \cdot b \cdot \bar{c}_i + a \cdot \bar{b} \cdot \bar{c}_i \\
 &= (\bar{a} \cdot \bar{b} + a \cdot b) \cdot c_i + (\bar{a} \cdot b + a \cdot \bar{b}) \cdot \bar{c}_i \\
 &= (\bar{a} \oplus b) \cdot c_i + (a \oplus b) \cdot \bar{c}_i \\
 &= (a \oplus b) \oplus c_i
 \end{aligned}$$


Full Adder

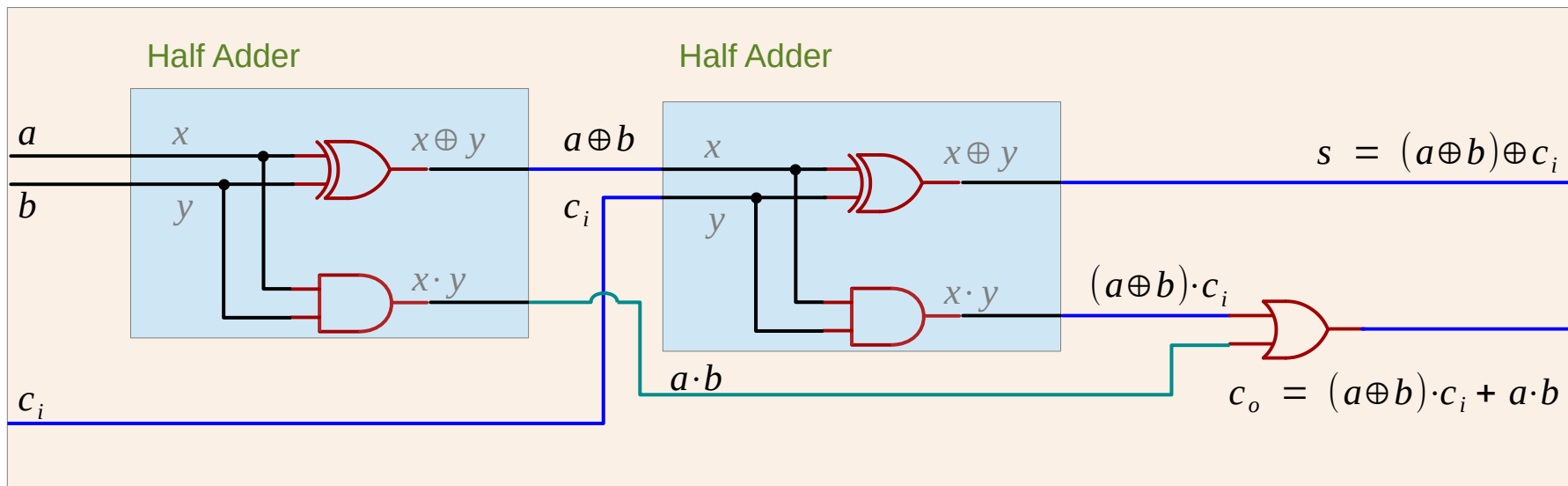

Full Adders and Half Adders

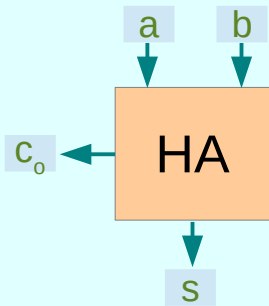


$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$	$\begin{array}{r} 1 \\ + 0 \\ \hline 01 \end{array}$	$\begin{array}{r} 0 \\ + 1 \\ \hline 01 \end{array}$	$\begin{array}{r} 0 \\ + 0 \\ \hline 00 \end{array}$
--	--	--	--

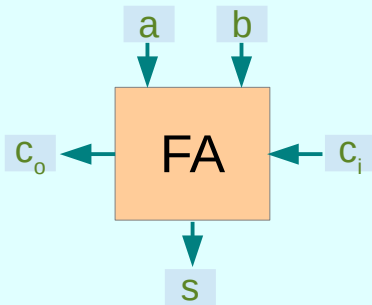

$\begin{array}{r} 0 \\ 0 \\ + 0 \\ \hline 00 \end{array}$	$\begin{array}{r} 0 \\ 1 \\ + 0 \\ \hline 01 \end{array}$	$\begin{array}{r} 1 \\ 0 \\ + 0 \\ \hline 01 \end{array}$	$\begin{array}{r} 1 \\ 1 \\ + 0 \\ \hline 10 \end{array}$
$\begin{array}{r} 0 \\ 0 \\ + 1 \\ \hline 01 \end{array}$	$\begin{array}{r} 0 \\ 1 \\ + 1 \\ \hline 10 \end{array}$	$\begin{array}{r} 1 \\ 0 \\ + 1 \\ \hline 10 \end{array}$	$\begin{array}{r} 1 \\ 1 \\ + 1 \\ \hline 11 \end{array}$

Truth Table

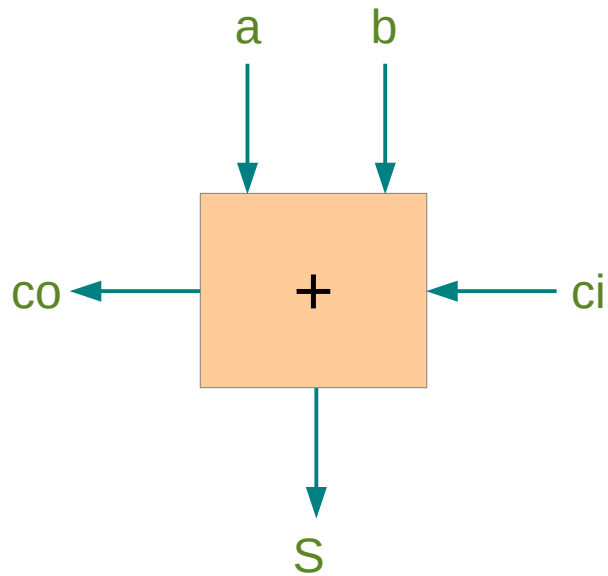

$$\begin{array}{r} a \\ b \\ + \quad ci \\ \hline co \end{array}$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

inputs output

Truth Table

References

[1] <http://en.wikipedia.org/>