

Carry Lookahead Adder (2A)

-
-

Copyright (c) 2025 - 2013 Young W. Lim.


Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


Carry Kill, Propagate, Generate conditions (1)

X	Y		
0	0	K	Kill ($=\overline{P}G$)
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

 


<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>

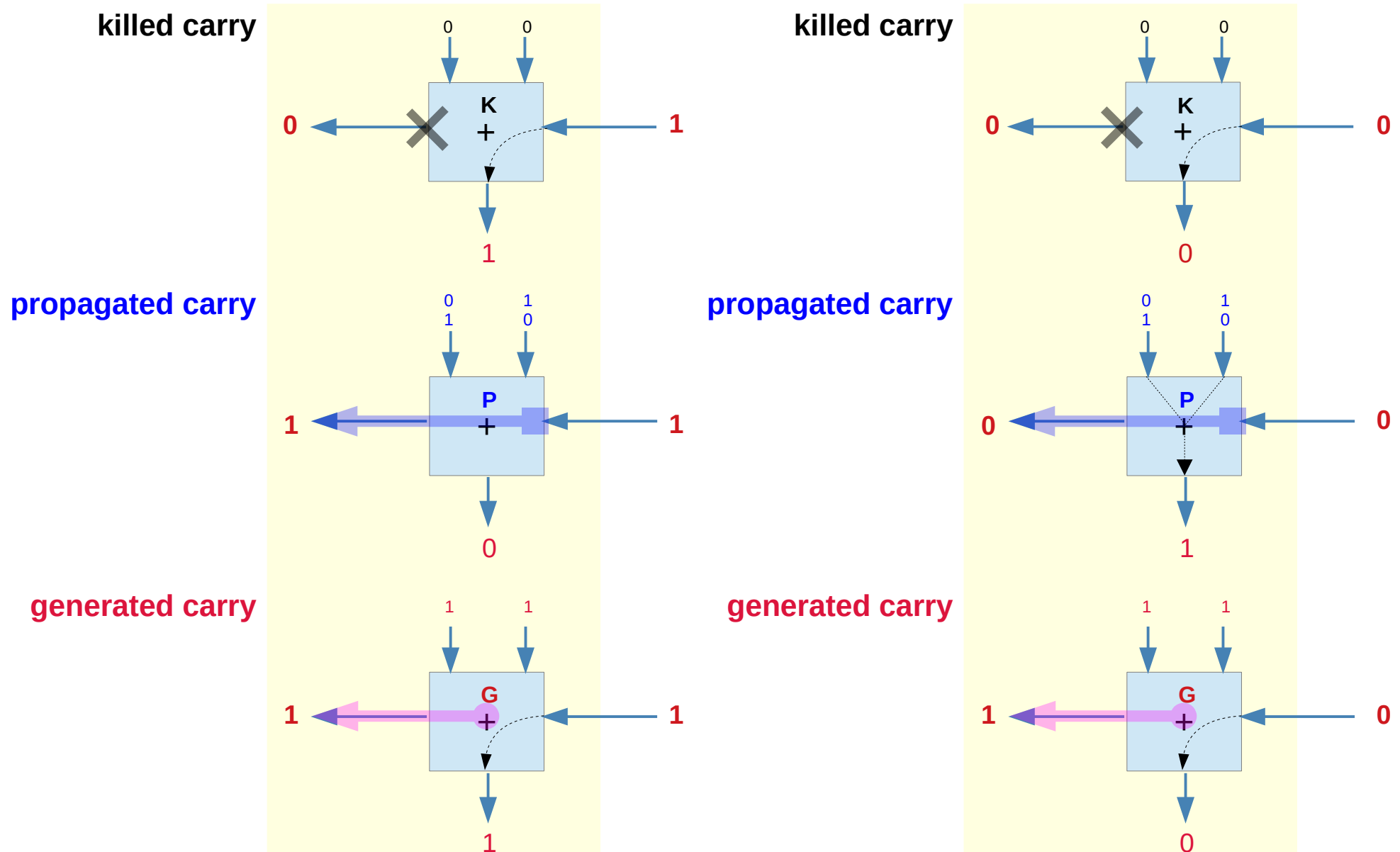Carry Kill, Propagate, Generate conditions (2)




C₀ propagation condition

 

$$s = p_3 \wedge p_2 \wedge p_1 \wedge p_0$$


$$= (a_3 \oplus b_3) \wedge (a_2 \oplus b_2) \wedge (a_1 \oplus b_1) \wedge (a_0 \oplus b_0)$$

 c₀ can be propagated to c_{out}
only if $s = 1$




https://en.wikipedia.org/wiki/Carry-skip_adder

A FA in terms of **p** and **g**

 

Half Adder	
$S = a \oplus b$	
$C = a \wedge b$	


a	b	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Full adder with additional generate and propagate signals.


https://en.wikipedia.org/wiki/Carry-skip_adder

Carry Equations in a Ripple Carry Adder

 

https://en.wikipedia.org/wiki/Carry-skip_adder

A 4-bit Ripple Carry Adder

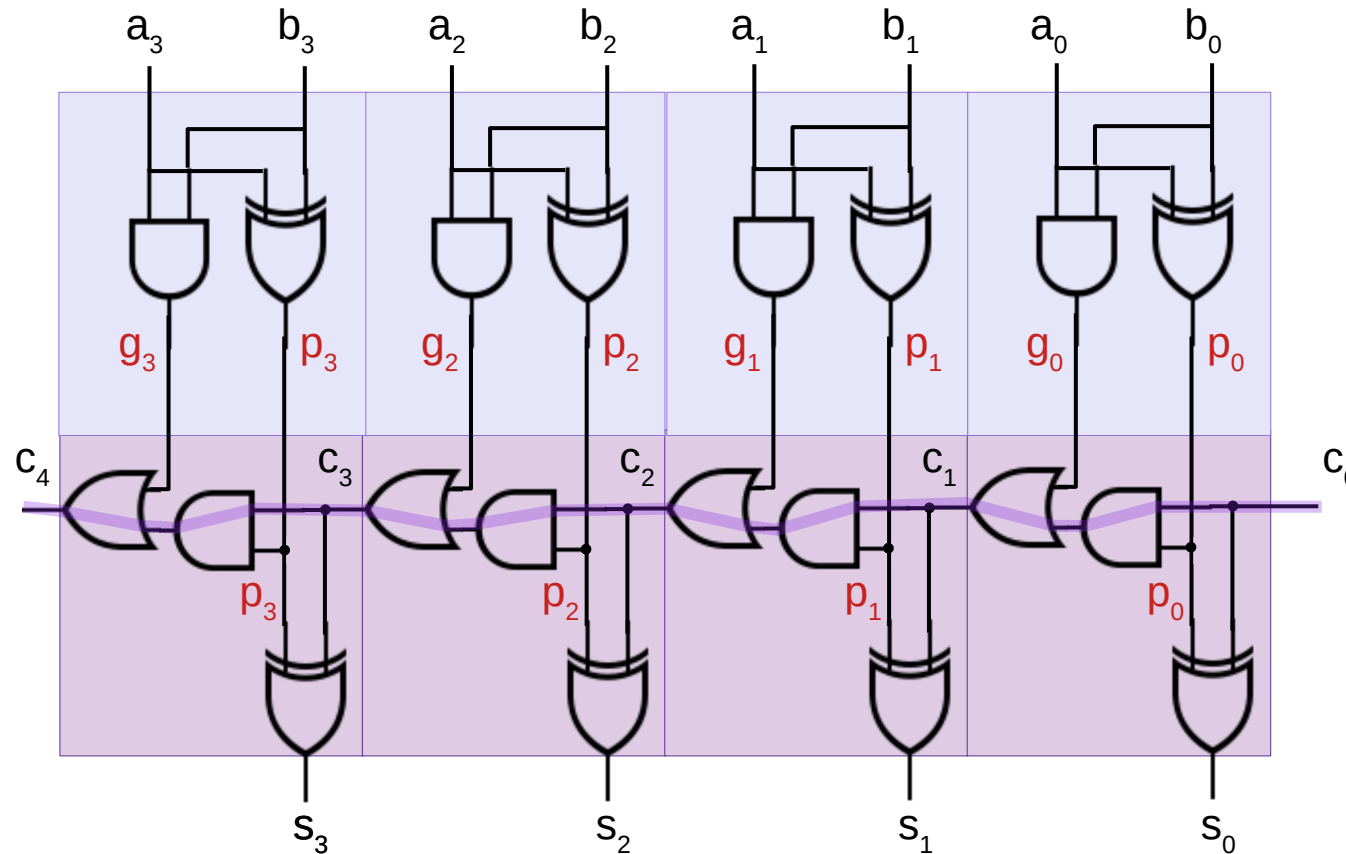

Half Adder 1

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$

Half Adder 2

$$c_{i+1} = g_i + p_i \wedge c_i$$

$$s_i = p_i \oplus c_i$$

Critical Path : $c_4 - c_3 - c_2 - c_1 - c_0$: 8 gate delay

<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

Expanding carry equations

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0 \quad \rightarrow \quad c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 c_1 \quad \rightarrow \quad c_2 = g_1 + p_1 [g_0 + p_0 c_0]$$

$$c_3 = g_2 + p_2 c_2 \quad \rightarrow \quad c_3 = g_2 + p_2 [g_1 + p_1 [g_0 + p_0 c_0]]$$

$$c_4 = g_3 + p_3 c_3 \quad \rightarrow \quad c_4 = g_3 + p_3 [g_2 + p_2 [g_1 + p_1 [g_0 + p_0 c_0]]]$$


c_{out}

c_{in}

 


$$\begin{aligned} g_0 + p_0 c_0 &= c_1 \\ g_1 + p_1 g_0 + p_1 p_0 c_0 &= c_2 \\ g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0 &= c_3 \\ g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0 &= c_4 \end{aligned}$$

 Carry Generate and Carry Propagate Signals



 
*these carries can
be computed in parallel*



Carry equations into Gates (1)

$$c_{i+1} = g_i + p_i c_i$$
 
$$c_4 = g_3 + p_3 [g_2 + p_2 [g_1 + p_1 [g_0 + p_0 c_0]]]$$



8 gate delay

Fan-in number: small
Stage number: large

Ripple Carry Adder

Carry equations into Gates (2)


$g_3 +$
$p_3 g_2 +$
$p_3 p_2 g_1 +$
$p_3 p_2 p_1 g_0 +$
$p_3 p_2 p_1 p_0 c_0$

$$g_0 + p_0 c_0 = c_1$$


$$g_1 + p_1 g_0 + p_1 p_0 c_0 = c_2$$

$$g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0 = c_3$$

 
$$g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0 = c_4$$



Sum of Product :
2 gate delay

 


Fan-in number: large
Stage number: small

 


Carry Lookahead Adder

Carry Lookahead Adder

 


Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

Carry Lookahead Adder

 

Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

Replicating carry circuits (1)

 

Half Adder

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$


Half Adder

$$C_{i+1} = g_i + p_i \wedge C_i$$

$$S_i = p_i \oplus C_i$$

*no merit
in reducing
a critical path delay*




Replicating carry circuits (2)

 

*Sum of Product :
2 gate delay*

*c_i 's can be computed
in parallel*

   *since g_i 's and p_i 's
are computed in parallel*



Limitations of Carry Lookahead


AND ₂ , OR ₂		$g_0 + p_0 c_0 = c_1$
AND ₃ , OR ₃		$g_1 + p_1 g_0 + p_1 p_0 c_0 = c_2$
AND ₄ , OR ₄		$g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0 = c_3$
AND ₅ , OR ₅		$g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0 = c_4$
⋮	⋮	
AND ₃₂ , OR ₃₂	possible?	$= c_{31}$
AND ₃₃ , OR ₃₃	possible?	$= c_{32}$

Large number of fan-in : impractical




{ High Radix Addition (2^9)
 Multi-level Carry Lookahead





A 4-bit Carry Lookahead Adder

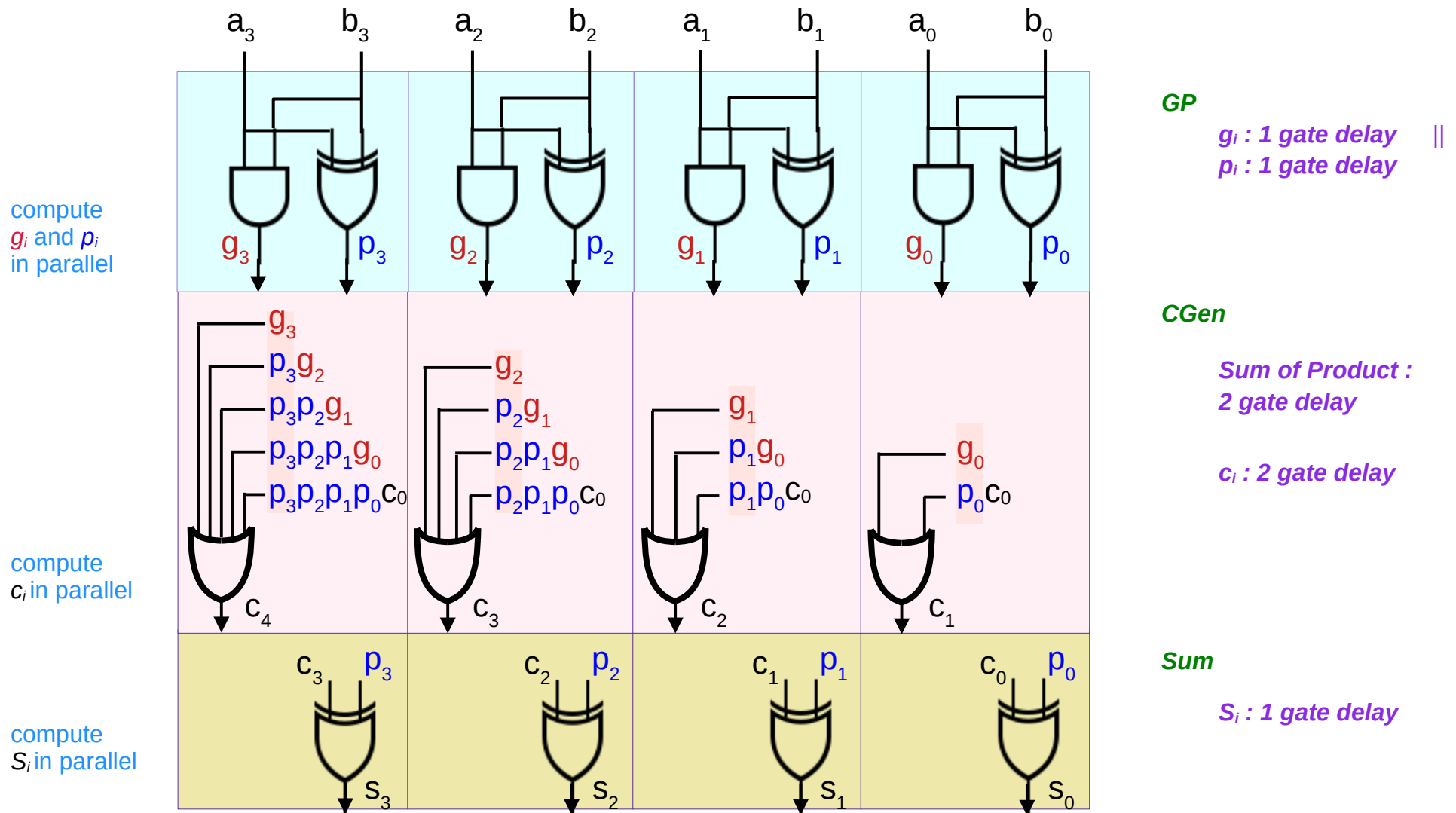


A 16-bit adder using four 4-bit CLA's

 

    partition a 16-bit adder into four 4-bit **CLA** blocks : B3, B2, B1, B0



Block CLA Structures (1)

 

Block CLA Structures (2)


Each block computes 4 **g**'s and 4 **p**'s in parallel

As soon as c_{in} , 4 **g**'s, and 4 **p**'s of each block is available,
each block computes 4 carries in parallel


As soon as 4 carries and 4 **p**'s of each block is available,
each block computes 4 sums in parallel

However,
only after c_{out} of B0/B1/B2 is available,
the four carries of B1/B2/B3 can be computed

 These can be computed in parallel,
if block carry generate signal G_{Bi}
and block carry propagate signal P_{Bi}
are used




Multi-level CLA

 

Block Carry Equations

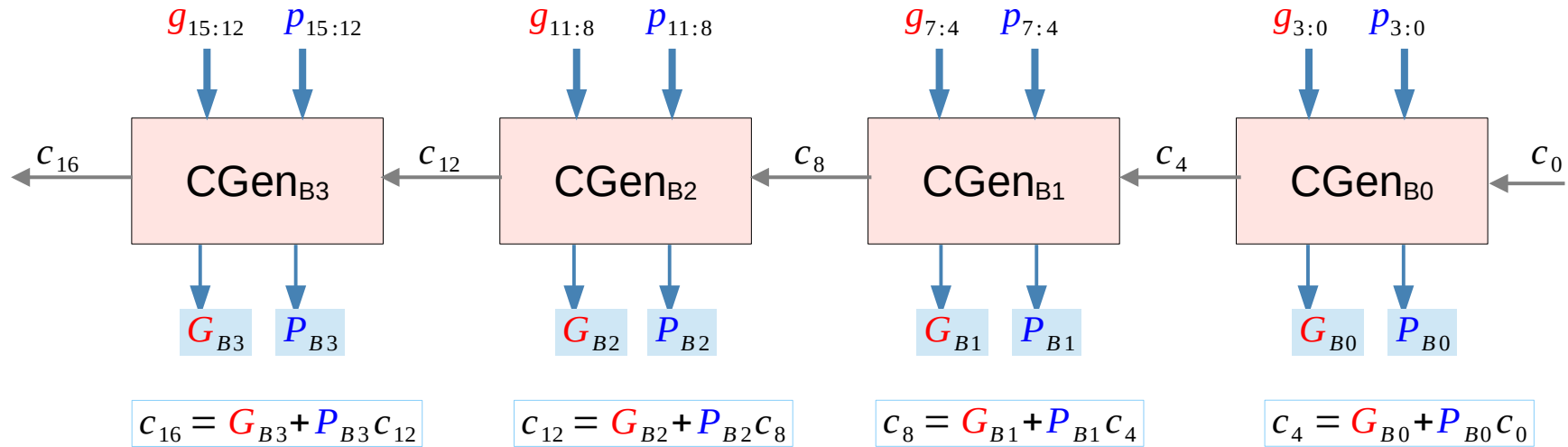Let us focus on the carry circuits of each block




Define block G and block P signal to compute c_{16} , c_{12} , c_8 , c_4 in parallel

G_{Bi} denotes the carries
which are generated in the block Bi

$P_{Bi}c_{in}$ denotes the input carry c_{in}
which is propagated through the block Bi

 Block Carry Generate and Propagate Signals



Expanding Block Carry Equations

$$C_{4 \cdot (i+1)} = G_{Bi} + P_{Bi} C_{4 \cdot i}$$

$$C_4 = G_{B0} + P_{B0} C_0 \quad \rightarrow \quad C_4 = G_{B0} + P_{B0} C_0$$


$$C_8 = G_{B1} + P_{B1} C_4 \quad \rightarrow \quad C_8 = G_{B1} + P_{B1} [G_{B0} + P_{B0} C_0]$$

$$C_{12} = G_{B2} + P_{B2} C_8 \quad \rightarrow \quad C_{12} = G_{B2} + P_{B2} [G_{B1} + P_{B1} [G_{B0} + P_{B0} C_0]]$$

$$C_{16} = G_{B3} + P_{B3} C_{12} \quad \rightarrow \quad C_{16} = G_{B3} + P_{B3} [G_{B2} + P_{B2} [G_{B1} + P_{B1} [G_{B0} + P_{B0} C_0]]]$$


C_{out}

C_{in}

 


$$\begin{aligned} G_{B0} + P_{B0} C_0 &= C_4 \\ G_{B1} + P_{B1} G_{B0} + P_{B1} P_{B0} C_0 &= C_8 \\ G_{B2} + P_{B2} G_{B1} + P_{B2} P_{B1} G_{B0} + P_{B2} P_{B1} P_{B0} C_0 &= C_{12} \\ G_{B3} + P_{B3} G_{B2} + P_{B3} P_{B2} G_{B1} + P_{B3} P_{B2} P_{B1} G_{B0} + P_{B3} P_{B2} P_{B1} P_{B0} C_0 &= C_{16} \end{aligned}$$

Block Carry Generating Circuits

 

Carry Lookahead Logic Comparison

$$C_{i+1} = g_i + p_i C_i$$

 

Block B0 Carries


$$g_0 + p_0 C_0 = C_1$$

$$g_1 + p_1 g_0 + p_1 p_0 C_0 = C_2$$

$$g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 C_0 = C_3$$

$$g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0 = C_4$$
 
$$C_{4 \cdot (i+1)} = G_{Bi} + P_{Bi} C_{4 \cdot i}$$



Group G0 Carries

$$G_{B0} + P_{B0} C_0 = C_4$$

$$G_{B1} + P_{B1} G_{B0} + P_{B1} P_{B0} C_0 = C_8$$


$$G_{B2} + P_{B2} G_{B1} + P_{B2} P_{B1} G_{B0} + P_{B2} P_{B1} P_{B0} C_0 = C_{12}$$

$$G_{B3} + P_{B3} G_{B2} + P_{B3} P_{B2} G_{B1} + P_{B3} P_{B2} P_{B1} G_{B0} + P_{B3} P_{B2} P_{B1} P_{B0} C_0 = C_{16}$$

the same structure

Block Carry Generating Circuits – simplified

 
Let us focus on the carry circuits of each block



has the same structure as the structure of each block

$$\begin{aligned}
 G_{B0} + P_{B0}c_0 &= c_4 \\
 G_{B1} + P_{B1}G_{B0} + P_{B1}P_{B0}c_0 &= c_8 \\
 G_{B2} + P_{B2}G_{B1} + P_{B2}P_{B1}G_{B0} + P_{B2}P_{B1}P_{B0}c_0 &= c_{12} \\
 G_{B3} + P_{B3}G_{B2} + P_{B3}P_{B2}G_{B1} + P_{B3}P_{B2}P_{B1}G_{B0} + P_{B3}P_{B2}P_{B1}P_{B0}c_0 &= c_{16}
 \end{aligned}$$

 G_{B0}, P_{B0} : Block Carry Generate and Propagate




$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$

$$G_{B0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$



$$P_{B0} = p_3 p_2 p_1 p_0$$

$$c_4 = G_{B0} + P_{B0} c_0$$

 


G_{B0} denotes the generated carries in the block B0

 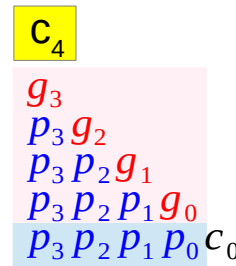$P_{B0} c_0$ denotes the the propagated input carry c_0



 G_{B1}, P_{B1} : Block Carry Generate and Propagate




$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 + p_7 p_6 p_5 p_4 c_4$$

$$G_{B1} = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$


$$P_{B1} = p_7 p_6 p_5 p_4$$

$$c_8 = G_{B1} + P_{B1} c_4$$

 


G_{B1} denotes the generated carries in the block B1


 
$P_{B1} c_4$ denotes the the propagated input carry c_4



 G_{B2}, P_{B2} : Block Carry Generate and Propagate



  G_{B3}, P_{B3} : Block Carry Generate and Propagate




$$c_{16} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} + p_{15}p_{14}p_{13}p_{12}c_{12}$$

$$G_{B3} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12}$$

$$P_{B3} = p_{15}p_{14}p_{13}p_{12}$$


$$c_{16} = G_{B3} + P_{B3}c_{12}$$

 


G_{B3} denotes the generated carries in the block B3

$P_{B2}c_8$ denotes the the propagated input carry c_8

 
Block Carry Generating Circuits – detailed




Simple Carry Lookahead Adder – B0

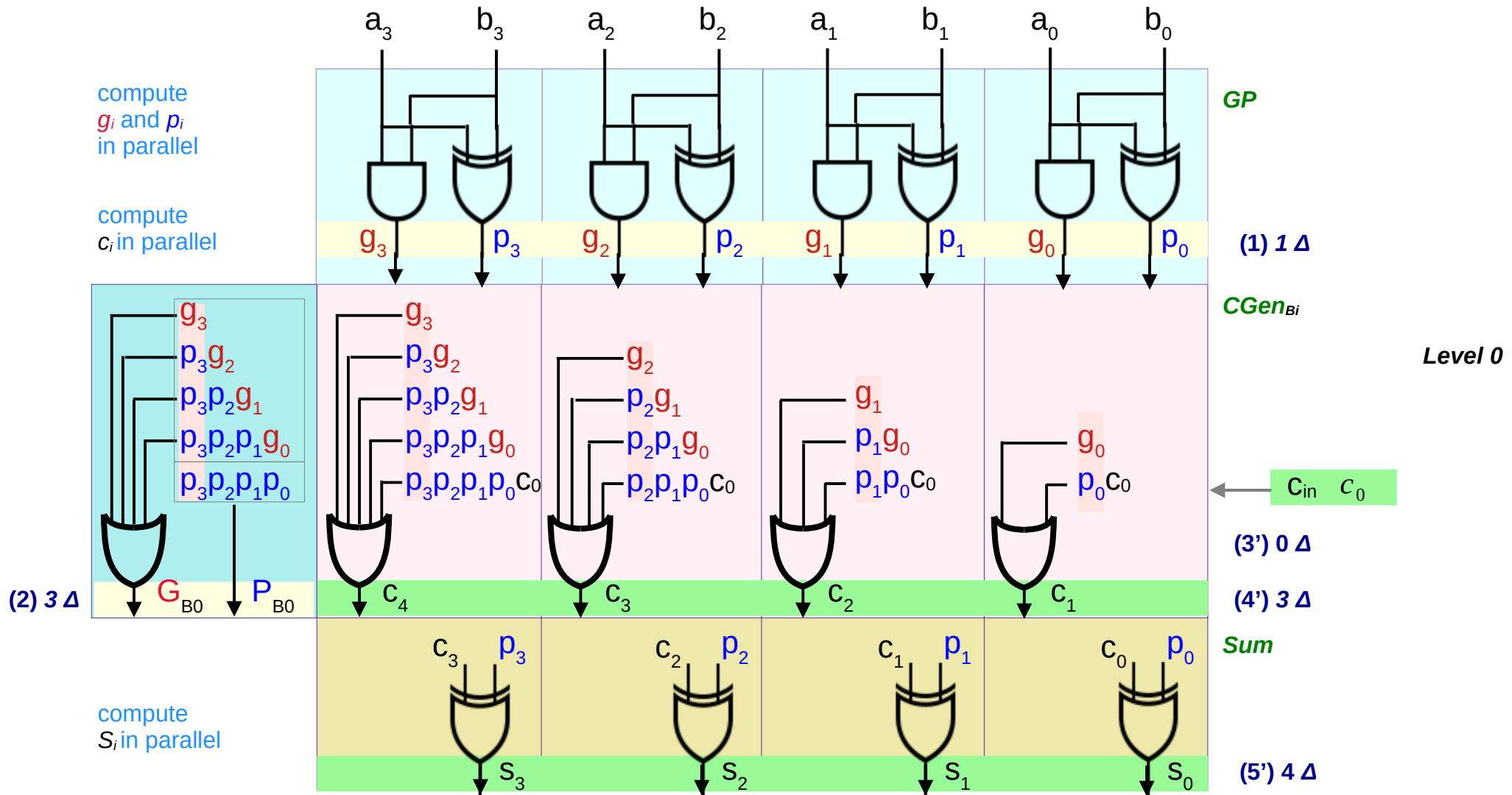


Simple Carry Lookahead Adder – B1

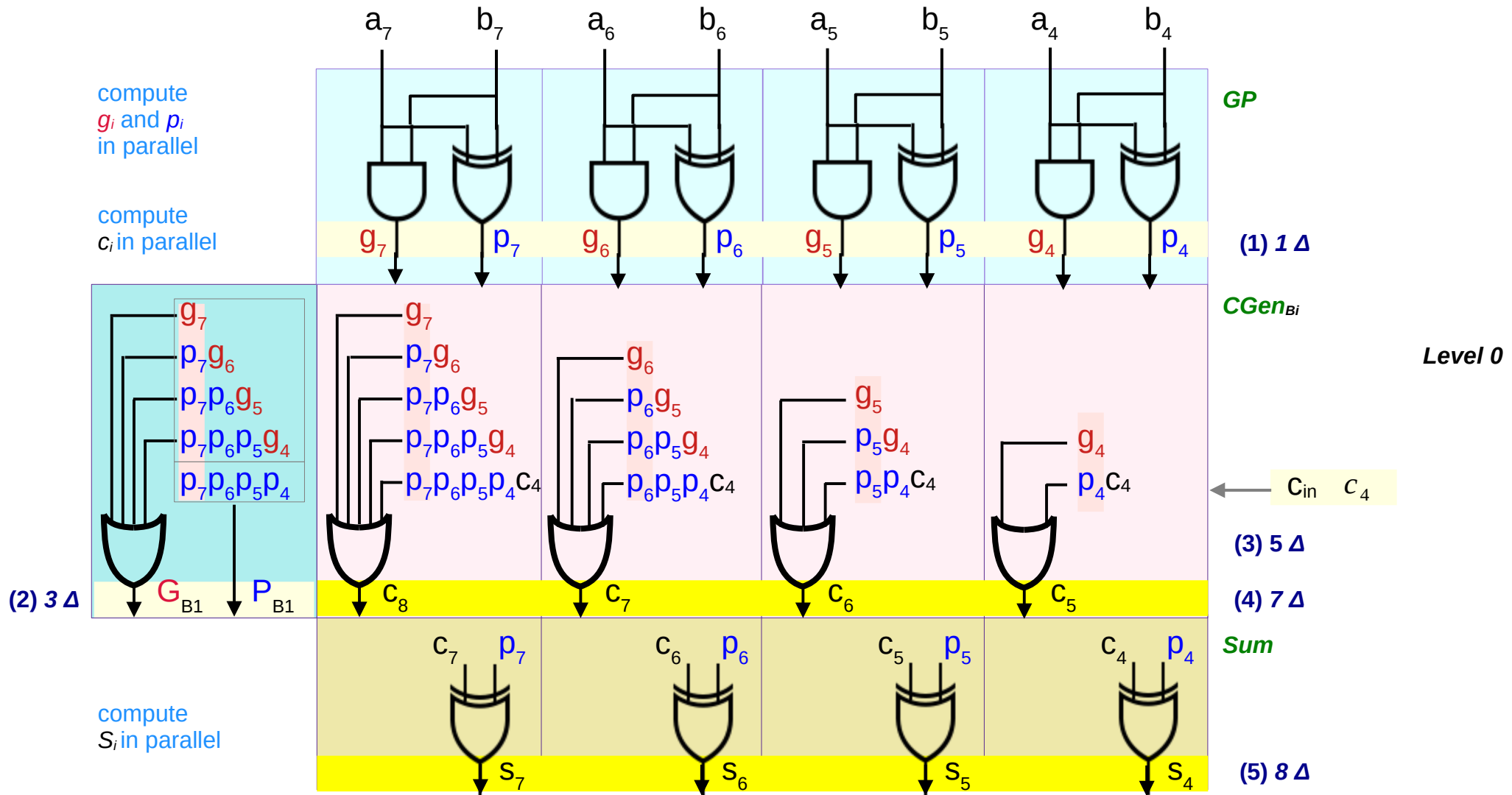


Simple Carry Lookahead Adder – B2

 


Simple Carry Lookahead Adder – B3

 

 A 2-Level Carry Lookahead Adder – Level 1



Delay calculations of 2-Level CLA (1)

 

Delay calculations of 2-Level CLA (2)

Starting at time of zero:

- calculation of p_i and g_i is done at time 1,
- calculation of the P_{Bi} is done at time 2,
- calculation of the G_{Bi} is done at time 3,
- calculation of the inputs for the $CGen_{Bi}$ from the $CGen_{G0}$ are done at:
 - time 0 for $CGen_{B0}$,
 - time 5 for $CGen_{B1}$, $CGen_{B2}$, $CGen_{B3}$,
- calculation of the S_i are done at:
 - time 4 for Sum_{B0} ,
 - time 8 for Sum_{B1} , Sum_{B2} , Sum_{B3} ,
- calculation of the final carry bit (C_{16}) is done at time 5.

The maximal time is 8 gate delays (for $S_{[4:15]}$).


https://en.wikipedia.org/wiki/Carry-lookahead_adder

A Variation of 2 Level CLA

Ripple Carry Adder + Block Carry Lookahead

S. & D. Harris, Digital Design and Computer Architecture 2nd ed.


A 4-bit Ripple Carry Adder

 

Critical Path : $c_4 - c_3 - c_2 - c_1 - c_0$: 8 gate delay


<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

A 16-bit adder using four 4-bit CLA's

 


A 4-bit Ripple Carry Adder
 
$$C_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0$$



carry paths
in the 4 FA's

 

carry lookahead
circuits


$$C_4 = G_{B0} + P_{B0} C_0$$

$$G_{B0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$


$$P_{B0} = p_3 p_2 p_1 p_0$$

A 4-bit Ripple Carry Adder

 the path delay from c_{in} to c_{out} : 8 gate delay



carry paths
in the 4 FA's

 


carry lookahead
circuits

the path delay from c_{in} to c_{out} : 2 gate delay

C_{out}	C_{in}
C_4	C_0
C_8	C_4
C_{12}	C_8
C_{16}	C_{12}

 
G_{B0}, P_{B0} : Block Carry Generate and Propagate



$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$

$$G_{B0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$P_{B0} = p_3 p_2 p_1 p_0$$

 

$$c_4 = G_{B0} + P_{B0} c_0$$

$$G_{B0} \leftarrow g_0 : 6\Delta$$

$$G_{B0} \leftarrow g_1 : 5\Delta$$

$$G_{B0} \leftarrow g_2 : 3\Delta$$

$$G_{B0} \leftarrow g_3 : 1\Delta$$

$$G_{B0} \leftarrow p_1 : 6\Delta$$

$$G_{B0} \leftarrow p_2 : 4\Delta$$

$$G_{B0} \leftarrow p_3 : 2\Delta$$

$$P_{B0} \leftarrow p_0 : 1\Delta$$

$$P_{B0} \leftarrow p_1 : 1\Delta$$

$$P_{B0} \leftarrow p_2 : 1\Delta$$

$$P_{B0} \leftarrow p_3 : 1\Delta$$

$$\text{delay}(c_4 \leftarrow g_i) \leq 7\Delta$$

$$\text{delay}(c_4 \leftarrow p_i) = 3\Delta$$


$$\text{delay}(c_4 \leftarrow c_0) = 2\Delta$$

$$\text{delay}(G_{B0} \leftarrow g_i) \leq 6\Delta$$

$$\text{delay}(G_{B0} \leftarrow p_i) \leq 6\Delta$$

$$\text{delay}(P_{B0} \leftarrow p_i) = 1\Delta$$

 G_{B1}, P_{B1} : Block Carry Generate and Propagate




$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 + p_7 p_6 p_5 p_4 c_4$$

$$G_{B1} = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$

$$P_{B1} = p_7 p_6 p_5 p_4$$

$$c_8 = G_{B1} + P_{B1} c_4$$

 

$$G_{B1} \leftarrow g_7 : 6\Delta$$

$$G_{B1} \leftarrow g_6 : 5\Delta$$

$$G_{B1} \leftarrow g_5 : 3\Delta$$

$$G_{B1} \leftarrow g_4 : 1\Delta$$

$$G_{B1} \leftarrow p_5 : 6\Delta$$

$$G_{B1} \leftarrow p_6 : 4\Delta$$

$$G_{B1} \leftarrow p_7 : 2\Delta$$

$$P_{B1} \leftarrow p_4 : 1\Delta$$

$$P_{B1} \leftarrow p_5 : 1\Delta$$

$$P_{B1} \leftarrow p_6 : 1\Delta$$

$$P_{B1} \leftarrow p_7 : 1\Delta$$

$$\text{delay}(c_8 \leftarrow g_i) \leq 7\Delta$$

$$\text{delay}(c_8 \leftarrow p_i) = 3\Delta$$



$$\text{delay}(c_8 \leftarrow c_4) = 2\Delta$$

$$\text{delay}(G_{B1} \leftarrow g_i) \leq 6\Delta$$

$$\text{delay}(G_{B1} \leftarrow p_i) \leq 6\Delta$$

$$\text{delay}(P_{B1} \leftarrow p_i) = 1\Delta$$

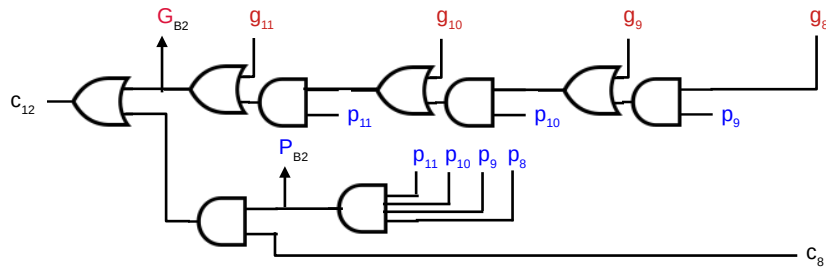 G_{B2}, P_{B2} : Block Carry Generate and Propagate



$$c_{12} = g_{11} + p_{11}g_{10} + p_{11}p_{10}g_9 + p_{11}p_{10}p_9g_8 + p_{11}p_{10}p_9p_8c_8$$

$$G_{B2} = g_{11} + p_{11}g_{10} + p_{11}p_{10}g_9 + p_{11}p_{10}p_9g_8$$



$$P_{B2} = p_{11}p_{10}p_9p_8$$

$$c_{12} = G_{B2} + P_{B2}c_8$$

$G_{B2} \leftarrow g_{11} : 6\Delta$		$P_{B2} \leftarrow p_8 : 1\Delta$
$G_{B2} \leftarrow g_{10} : 5\Delta$	$G_{B2} \leftarrow p_9 : 6\Delta$	$P_{B2} \leftarrow p_9 : 1\Delta$
$G_{B2} \leftarrow g_9 : 3\Delta$	$G_{B2} \leftarrow p_{10} : 4\Delta$	$P_{B2} \leftarrow p_{10} : 1\Delta$
$G_{B2} \leftarrow g_8 : 1\Delta$	$G_{B2} \leftarrow p_{11} : 2\Delta$	$P_{B2} \leftarrow p_{11} : 1\Delta$

$\text{delay}(c_{12} \leftarrow g_i) \leq 7\Delta$	$\text{delay}(G_{B2} \leftarrow g_i) \leq 6\Delta$
$\text{delay}(c_{12} \leftarrow p_i) = 3\Delta$	$\text{delay}(G_{B2} \leftarrow p_i) \leq 6\Delta$
$\text{delay}(c_{12} \leftarrow c_8) = 2\Delta$	$\text{delay}(P_{B2} \leftarrow p_i) = 1\Delta$

  G_{B3}, P_{B3} : Block Carry Generate and Propagate



$$c_{16} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} + p_{15}p_{14}p_{13}p_{12}c_{12}$$

$$G_{B3} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12}$$


$$P_{B3} = p_{15}p_{14}p_{13}p_{12}$$

$$c_{16} = G_{B3} + P_{B3}c_{12}$$

$G_{B3} \leftarrow g_{15} : 6\Delta$		$P_{B3} \leftarrow p_{12} : 1\Delta$
$G_{B3} \leftarrow g_{14} : 5\Delta$	$G_{B3} \leftarrow p_{13} : 6\Delta$	$P_{B3} \leftarrow p_{13} : 1\Delta$
$G_{B3} \leftarrow g_{13} : 3\Delta$	$G_{B3} \leftarrow p_{14} : 4\Delta$	$P_{B3} \leftarrow p_{14} : 1\Delta$
$G_{B3} \leftarrow g_{12} : 1\Delta$	$G_{B3} \leftarrow p_{15} : 2\Delta$	$P_{B3} \leftarrow p_{15} : 1\Delta$

$delay(c_{16} \leftarrow g_i) \leq 7\Delta$	$delay(G_{B3} \leftarrow g_i) \leq 6\Delta$
$delay(c_{16} \leftarrow p_i) = 3\Delta$	$delay(G_{B3} \leftarrow p_i) \leq 6\Delta$
$delay(c_{16} \leftarrow c_{12}) = 2\Delta$	$delay(P_{B3} \leftarrow p_i) = 1\Delta$

Delay to generate all G_{Bi} and P_{Bi}

 

$$\begin{aligned}
 \text{delay}(p_i, g_i \leftarrow a_i, b_i) &= 1\Delta & \text{delay}(c_o \leftarrow G_{Bi}) &= 1\Delta \\
 \text{delay}(G_{Bi} \leftarrow p_i, g_i) &\leq 6\Delta & \text{delay}(c_o \leftarrow P_{Bi}) &= 2\Delta \\
 \text{delay}(P_{Bi} \leftarrow p_i, g_i) &= 1\Delta & \text{delay}(c_o \leftarrow c_i) &= 2\Delta
 \end{aligned}$$

$$\begin{aligned}
 \text{delay}(c_o \leftarrow a_i, b_i) &\leq 8\Delta \\
 \text{delay}(c_o \leftarrow a_i, b_i) &= 4\Delta \\
 \text{delay}(c_o \leftarrow c_i) &= 2\Delta
 \end{aligned}$$

p_i, g_i : all computed in parallel

T_{pg} : path delay from a_i, b_i to p_i, g_i 1Δ

T_{pg_block} : path delay from p_i, g_i to G_{Bi}, P_{Bi} 6Δ

$T_{pg} + T_{pg_block}$: path delay from a_i, b_i to G_{Bi}, P_{Bi} 7Δ

after $T_{pg} + T_{pg_block}$, all G_{bi} 's, P_{bi} 's are available.

But each carry lookahead circuit can compute its own c_{out} , only after c_{in} is ready.

Thus, $c_0 \rightarrow c_4 \rightarrow c_8 \rightarrow c_{12}$ forms a critical path

in the 1st block, the path delay $c_0 \rightarrow c_4$ takes T_{AND_OR}

in the 2nd block, the path delay $c_4 \rightarrow c_8$ takes T_{AND_OR}

in the 3rd block, the path delay $c_8 \rightarrow c_{12}$ takes T_{AND_OR}


in the 4th block, the path delay $c_{12} \rightarrow c_{16}$ takes T_{AND_OR}

	$C_{in} \rightarrow C_{out}$	<i>Path delay</i>
in the 1 st block,	$C_0 \rightarrow C_4$	$T_{AND_OR} = 2 \Delta$
in the 2 nd block,	$C_4 \rightarrow C_8$	$T_{AND_OR} = 2 \Delta$
in the 3 rd block,	$C_8 \rightarrow C_{12}$	$T_{AND_OR} = 2 \Delta$
in the 4 th block,	$C_{12} \rightarrow C_{16}$	$T_{AND_OR} = 2 \Delta$


	$C_0 \rightarrow C_{out}$	<i>Path delay</i>
in the 1 st block,	$C_0 \rightarrow C_4$	$T_{AND_OR} = 2 \Delta$
in the 2 nd block,	$C_0 \rightarrow C_8$	$T_{AND_OR} = 4 \Delta$
in the 3 rd block,	$C_0 \rightarrow C_{12}$	$T_{AND_OR} = 6 \Delta$
in the 4 th block,	$C_0 \rightarrow C_{16}$	$T_{AND_OR} = 8 \Delta$

A 4-bit Ripple Carry Adder

 While the carry lookahead operation is performed, the sum bits are computed by a ripple carry adder



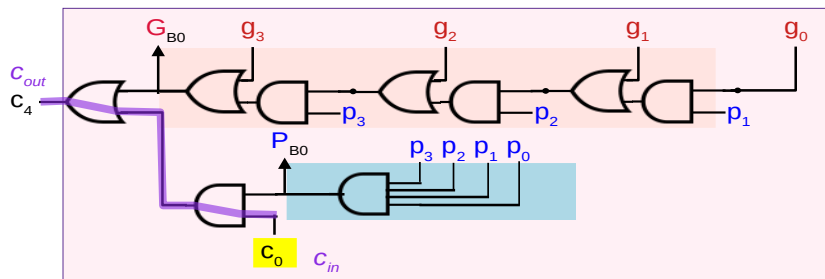$k = 4$ Full Adders $\rightarrow$ a 4-bit ripple carry adder



carry lookahead circuit

T_{pg} , T_{pg_block}

*While carry lookahead operation is performed,
the sum bits are computed by a ripple carry adder*


*the 1st block's ripple carry adder
starts to compute its sum bits using c_0 after $T_{pg} + T_{pg_block}$*

*the 2nd block's ripple carry adder
starts to compute its sum bits using c_4 after $T_{pg} + T_{pg_block} + 1 \cdot T_{AND_OR}$*

*the 3rd block's ripple carry adder
starts to compute its sum bits using c_8 after $T_{pg} + T_{pg_block} + 2 \cdot T_{AND_OR}$*

*the 4th block's ripple carry adder
starts to compute its sum bits using c_{12} after $T_{pg} + T_{pg_block} + 3 \cdot T_{AND_OR}$*

Critical paths after 7 Δ

 

$$\begin{aligned} \text{delay}(p_i, g_i \leftarrow a_i, b_i) &= 1\Delta \\ \text{delay}(G_{Bi} \leftarrow p_i, g_i) &\leq 6\Delta \\ \text{delay}(P_{Bi} \leftarrow p_i, g_i) &= 1\Delta \end{aligned}$$

$$\begin{aligned} \text{delay}(c_o \leftarrow G_{Bi}) &= 1\Delta \\ \text{delay}(c_o \leftarrow P_{Bi}) &= 2\Delta \\ \text{delay}(c_o \leftarrow c_i) &= 2\Delta \end{aligned}$$


$$\begin{aligned} \text{delay}(c_o \leftarrow a_i, b_i) &\leq 8\Delta \\ \text{delay}(c_o \leftarrow a_i, b_i) &= 4\Delta \\ \text{delay}(c_o \leftarrow c_i) &= 2\Delta \end{aligned}$$

p_i, g_i : all computed in parallel

The diagram illustrates the propagation of a carry signal through four stages of a carry-lookahead adder. Each stage consists of a propagate block (yellow) and a generate block (orange). The stages are labeled with carry inputs C_{16} , C_{12} , C_8 , and C_4 , and carry outputs C_{12} , C_8 , C_4 , and C_0 . Each stage has a generate signal G and a propagate signal P . The diagrams show how the carry signal propagates through the logic blocks, with each stage adding a delay of 2Δ . The total delay for the carry signal to reach C_0 is $2\Delta + 2\Delta + 2\Delta + 2\Delta = (16/4 - 1)\Delta$.

$$\begin{aligned} \text{delay}(c_{4(i+1)} \leftarrow a_i, b_i) &\leq 8\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow a_i, b_i) &= 4\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow c_{4i}) &= 2\Delta \end{aligned}$$

Young W. Lim
6/30/25

 


$$\begin{aligned} \text{delay}(c_{4(i+1)} \leftarrow G_{Bi}) &= 1 \Delta \\ \text{delay}(c_{4(i+1)} \leftarrow B_{Bi}) &= 2 \Delta \\ \text{delay}(c_{4(i+1)} \leftarrow c_{4i}) &= 2 \Delta \end{aligned}$$

$$\begin{aligned} \text{delay}(G_{Bi} \leftarrow a_i, b_i) &\leq 7 \Delta \\ \text{delay}(B_{Bi} \leftarrow a_i, b_i) &= 2 \Delta \end{aligned}$$

$$\begin{aligned} \text{delay}(c_{4(i+1)} \leftarrow a_i, b_i) &\leq 8 \Delta \\ \text{delay}(c_{4(i+1)} \leftarrow a_i, b_i) &= 4 \Delta \\ \text{delay}(c_{4(i+1)} \leftarrow c_{4i}) &= 2 \Delta \end{aligned}$$

computed in serial


A 4-bit Ripple Carry Adder

 


Critical Path : $c_i - c_{i+1} - c_{i+2} - c_{i+3} - s_{i+3}$: 7 gate delay

<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

 P_{Bi} 's, G_{Bi} 's are computed in parallel




A 4-bit Ripple Carry Adder

 


<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>


4-bit CLA

 


Multi-level Carry Lookahead

 

Contiguous Multi-level Carry Lookahead

 

Carry Skip Adder

 

Any kill or generate condition results in divided (broken) critical paths

All FA's in R-2 groups must have the propagate condition